Introduction to Electricity and Electronics

Student Guide

Prepared by BLIS GLOBAL Robotics Department

Copyright @2024

Week 4: Hands-on Projects

IN this week other topics will be blocked and you will perform below experiments:

Experiment 1: Using a theory of Serial ana Parallel circuit make an ON/OFF switch Lamp

Experiment 2: Using a breadboard make a Serial and Parallel circuit using LED and resistor and power supply of 7.4 v

Experiment 3: connect 4 DC Motor in Parallel and run all of them in forward direction using a power supply of 7.4 v

Experiment 4: Make a transistor switch circuit