Introduction to Electricity and Electronics

Student Guide

Prepared by BLIS GLOBAL Robotics Department

Copyright @2024

Week 6: Battery Connection Experiment

Course Title: Battery Connection Experiment

Introduction

This laboratory course is designed to help you understand the basic concepts of battery connections. Batteries are essential components in many electronic devices, and understanding how to connect them properly is crucial for powering circuits. In this experiment, you'll explore different methods of connecting batteries and observe how they affect the overall voltage and current in a circuit.

Objectives

By the end of this experiment, you should be able to:

1. Understand the differences between series and parallel battery connections.
2. Measure the voltage and current in circuits with different battery configurations.
3. Recognize the practical applications of various battery connections in everyday electronic devices.

Materials Needed

- Two or more identical batteries (e.g., AA or AAA)
- Battery holders (if available)
- Multimeter (to measure voltage and current)
- Connecting wires
- Light bulb or resistor (as a load)
- Breadboard (optional)

Theory

Batteries provide electrical energy to circuits. The way batteries are connected in a circuit can affect the overall voltage and current.

Series Connection

- Description: In a series connection, the positive terminal of one battery is connected to the negative terminal of the next battery. This configuration increases the total voltage while the current remains the same as a single battery.
- Formula:
    - Total Voltage: Vtotal=V1+V2+⋯+VnV_{total} = V_1 + V_2 + \dots + V_nVtotal=V1+V2+⋯+Vn
    - Current: I=Same as individual battery currentI = \text{Same as individual battery current}I=Same as individual battery current

Parallel Connection

- Description: In a parallel connection, all the positive terminals of the batteries are connected together, and all the negative terminals are connected together. This configuration keeps the voltage the same as a single battery while increasing the total current.
- Formula:
    - Voltage: Vtotal=Same as individual battery voltageV_{total} = \text{Same as individual battery voltage}Vtotal=Same as individual battery voltage
    - Total Current: Itotal=I1+I2+⋯+InI_{total} = I_1 + I_2 + \dots + I_nItotal=I1+I2+⋯+In

---

Procedure

Part 1: Series Connection

1. Setup: Connect two or more batteries in series using connecting wires.
2. Measure Voltage: Use the multimeter to measure the total voltage across the series-connected batteries. Record your observations.
3. Connect Load: Connect the light bulb or resistor across the terminals of the series-connected batteries.
4. Observe Brightness: Observe the brightness of the light bulb. This indicates the total voltage applied.
5. Measure Current: Use the multimeter to measure the current flowing through the circuit. Record your observations.

Part 2: Parallel Connection

1. Setup: Connect the same batteries in parallel using connecting wires.

2. Measure Voltage: Use the multimeter to measure the total voltage across the parallel-connected batteries. Record your observations.
3. Connect Load: Connect the light bulb or resistor across the terminals of the parallel-connected batteries.
4. Observe Brightness: Observe the brightness of the light bulb. This indicates the voltage applied, which should be the same as a single battery.
5. Measure Current: Use the multimeter to measure the total current supplied by the parallel batteries. Record your observations.

Observations and Analysis

- Series Connection: Compare the measured voltage with the calculated total voltage. Analyze how the voltage increases with the number of batteries.
- Parallel Connection: Compare the current in the circuit with the calculated total current. Analyze how the current increases with the number of batteries while the voltage remains the same.
- Practical Applications: Discuss how these configurations are used in real-life applications, such as in flashlights (series) and battery banks (parallel).

Conclusion

This experiment demonstrated how different battery configurations can influence the behavior of electrical circuits. Understanding these connections is vital for designing and troubleshooting electronic devices that rely on battery power.

Safety Precautions

- Always handle batteries with care to avoid short circuits.
- Do not mix old and new batteries or batteries of different types in the same circuit.
- Ensure all connections are secure to prevent accidental disconnection during the experiment.

This concludes the laboratory course on Battery Connection Experiment.

4o